











## microphone

get close!

#### feedthru

### repeat



piezo transducer OR DIY speaker coil



 $8 \Omega$  speaker OR bone conductor OR jack to speaker OR



### on-board switches

rec (record) playE (play track once) playL (play while pressed)



gnd

10K default = 10 sec record time 500K pot to play w distorted sounds

3.3-5V





pins to external switches

playL ←→ vcc = play while pressed

any DIY on/off switch works

playE ←→ vcc = play once

rec ←→ vcc = record





#### mic input directly to speaker












# audio outputs

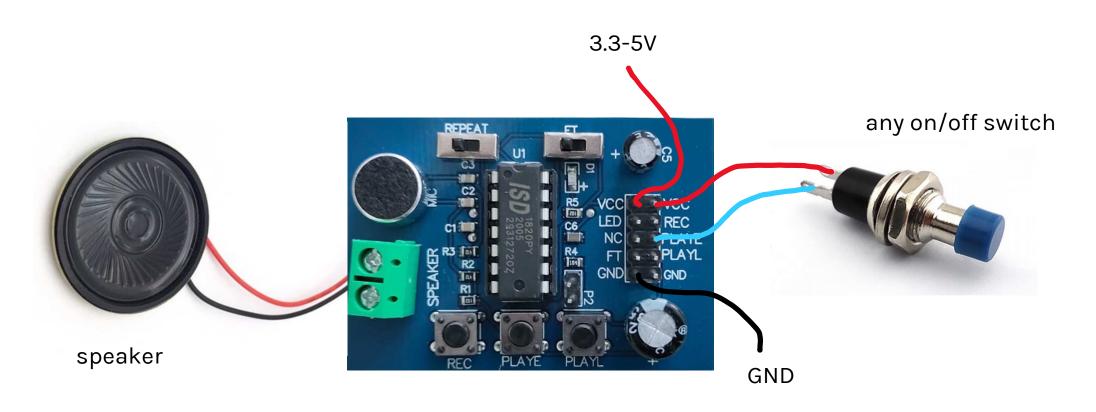

ISD1820 + 8 ohm speaker

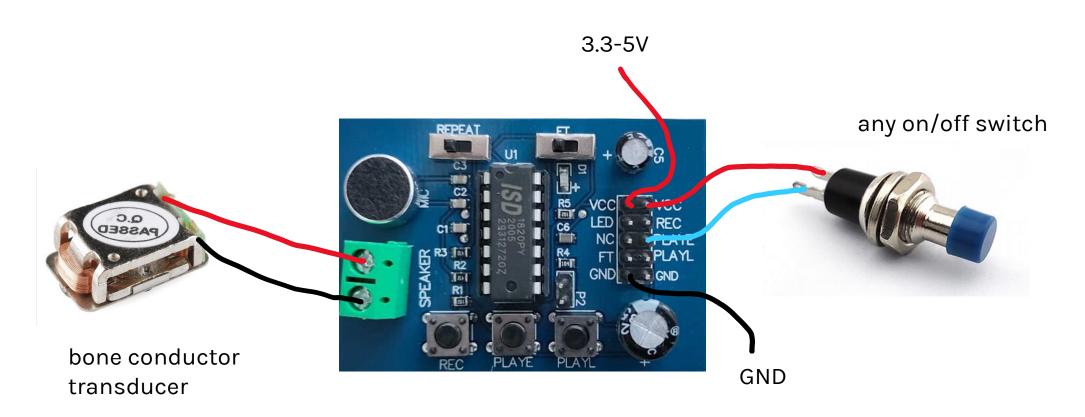

ISD1820 + bone conductor speaker

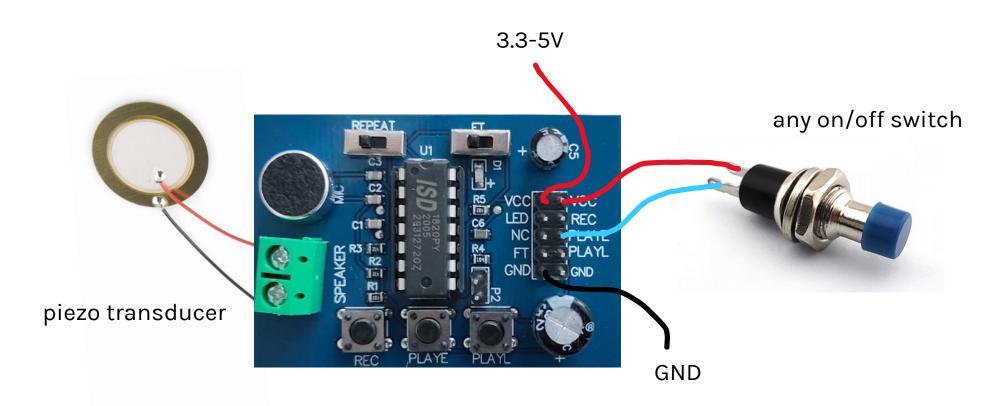

# ISD1820 + piezo speaker

Put between your teeth or on jawbone to hear sound

# distortion

3.3-5V

speaker (or other output device)






any on/off switch



default when jumper is used

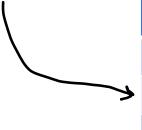

	Ω	Record time	Sample rate	Bandwidth
	80K	8 secs	8 KHz	3.4 KHz
>	100K	10 secs	6.4 KHz	2.6 KHz
	120K	12 secs	5.4 KHz	2.3 KHz
	160K	16 secs	4.0 KHz	1.7 KHz
	200K	20 secs	3.2KHz	1.3 KHz



250K or 500K potentiometer


ISD1820 + 500k pot

on p2: distorts the sound



speaker (or other output device)



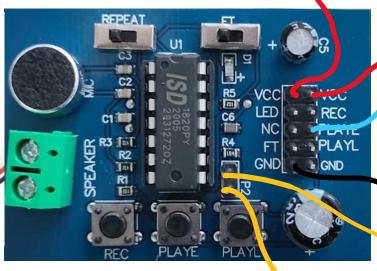

any on/off switch




### default when jumper is used

	Ω	Record time	Sample rate	Bandwidth
	80K	8 secs	8 KHz	3.4 KHz
×	100K	10 secs	6.4 KHz	2.6 KHz
	120K	12 secs	5.4 KHz	2.3 KHz
	160K	16 secs	4.0 KHz	1.7 KHz
	200K	20 secs	3.2KHz	1.3 KHz


0 Ω 50Κ Ω 100Κ Ω 200Κ Ω

# DIY variable resistor make with conductive paint


# triggers

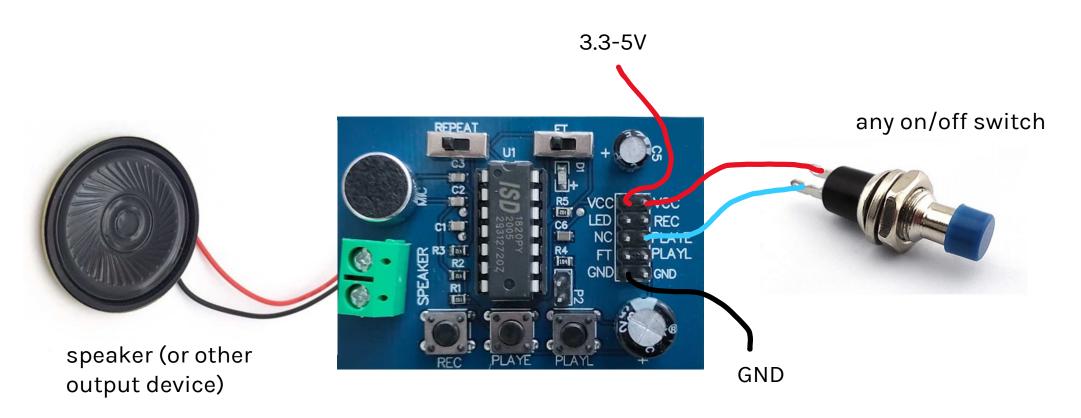

ISD1820 + light sensor

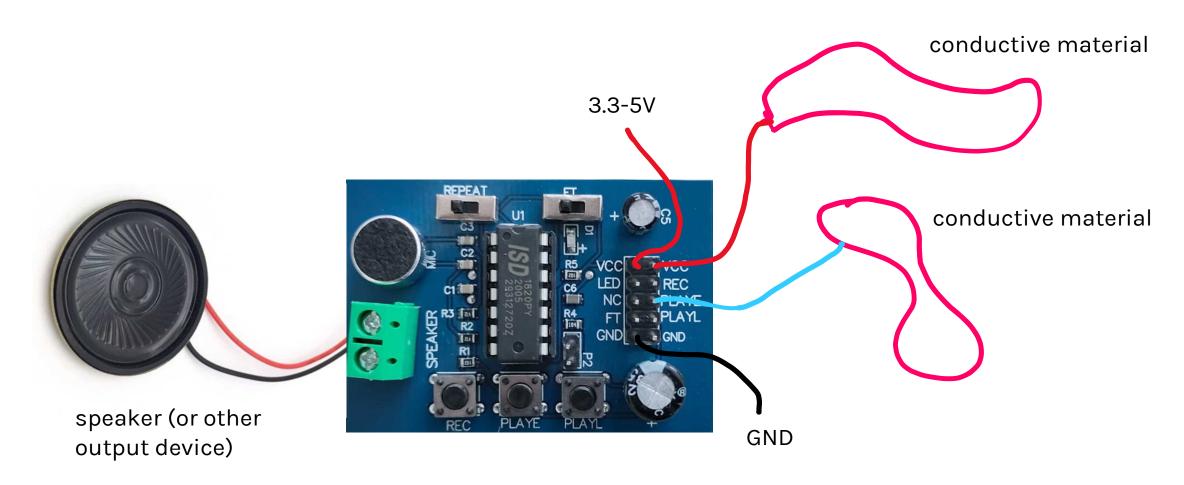


ISD1820 + light sensor

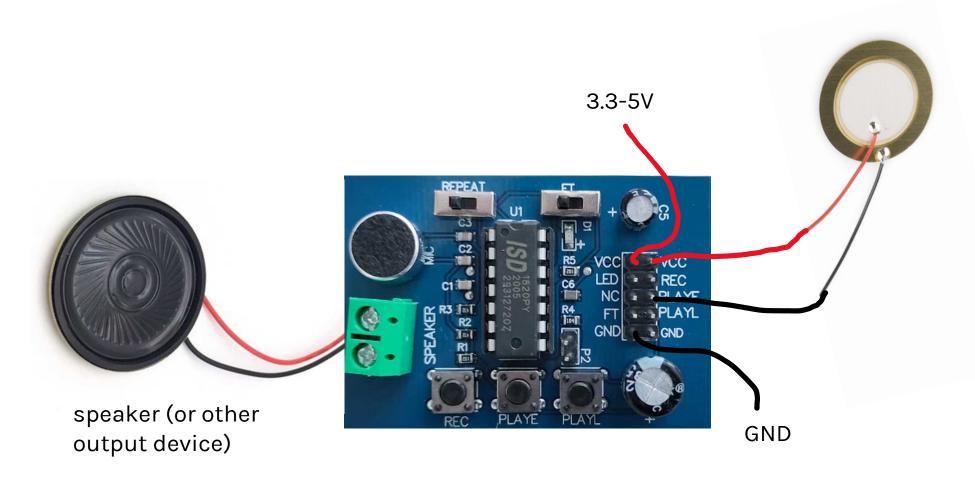


# ISD1820 + Piezo transducer

Press, bend or knock trigger

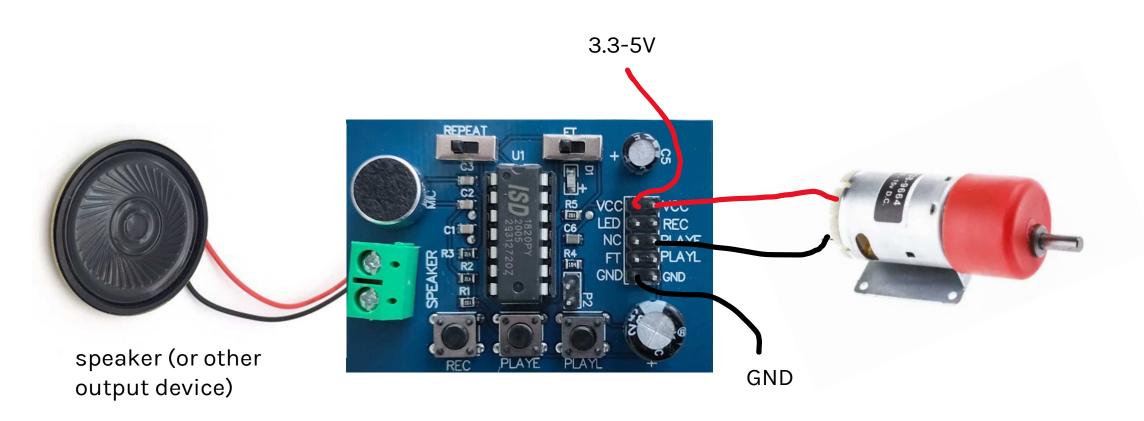


## ISD1820 + DC motor

Type e.g. 4.5-15V with gearbox

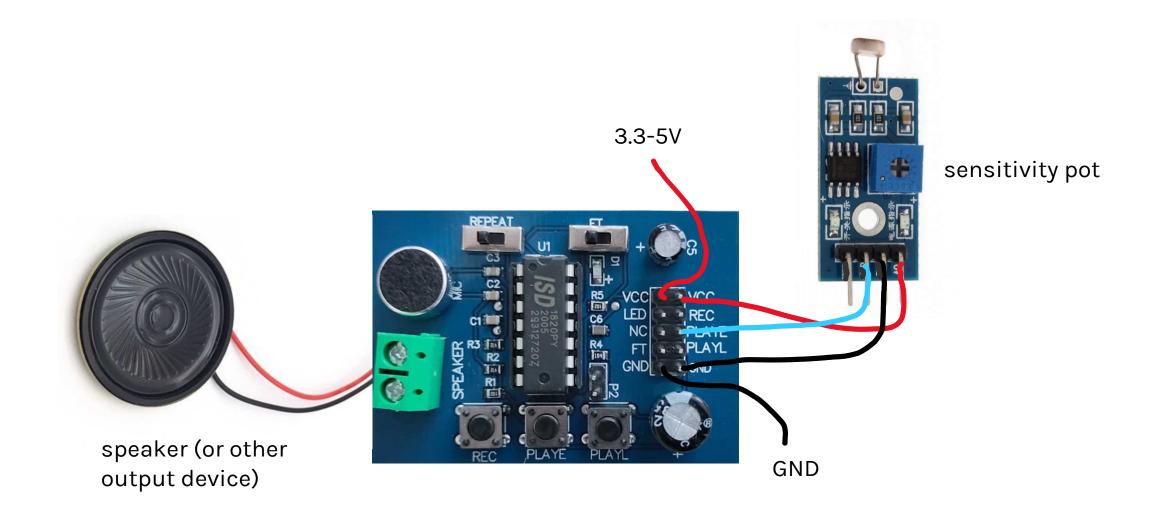


ISD1820 + light sensor

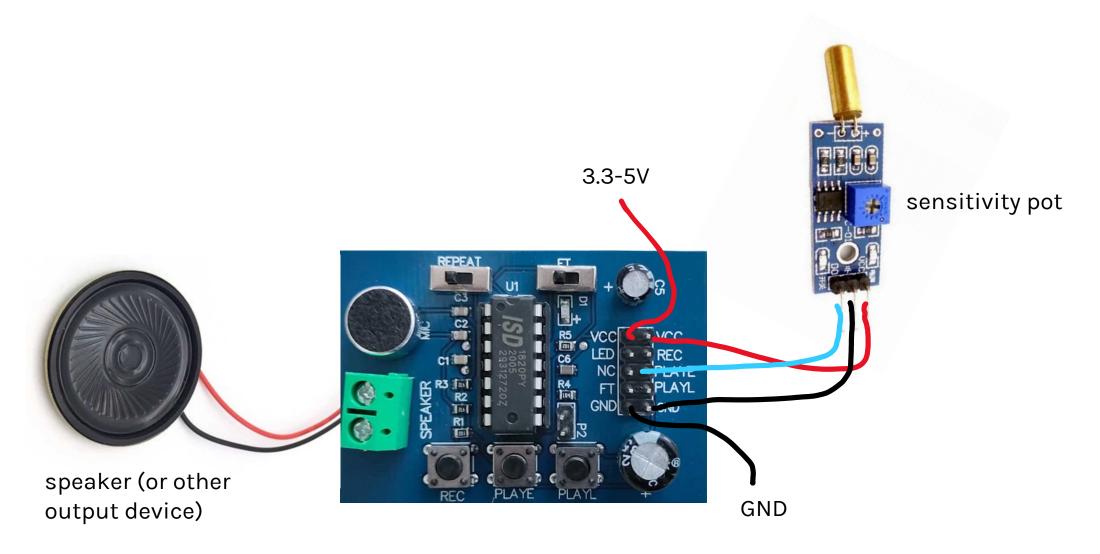


## ISD1820 + tilt switch


also useful as record switch!

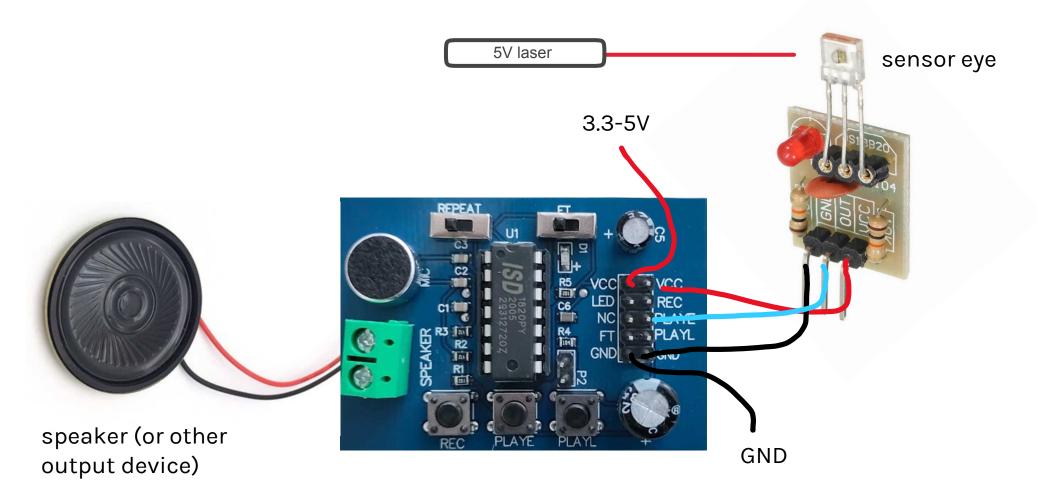


ISD1820 + red laser sensor

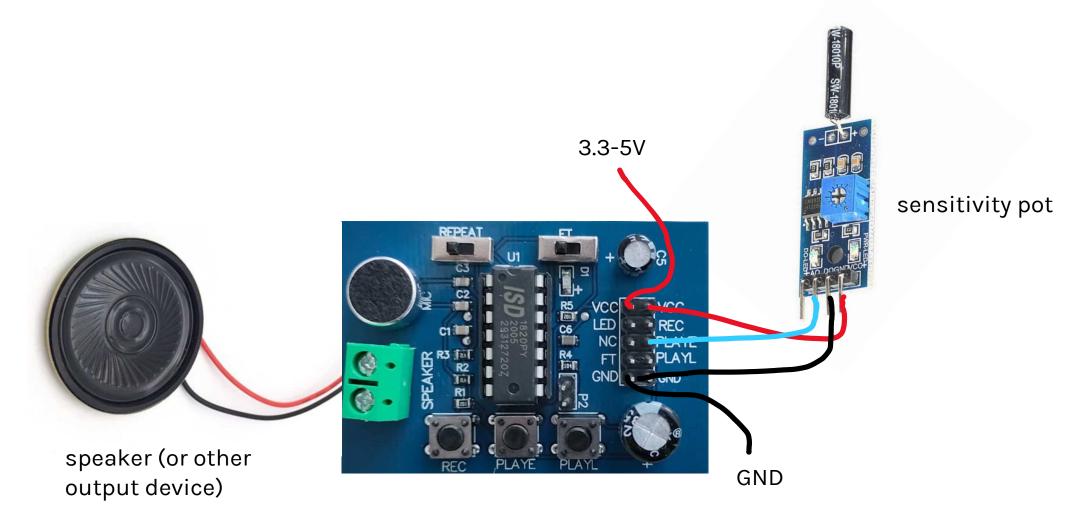


ISD1820 + vibration sensor

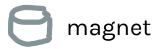


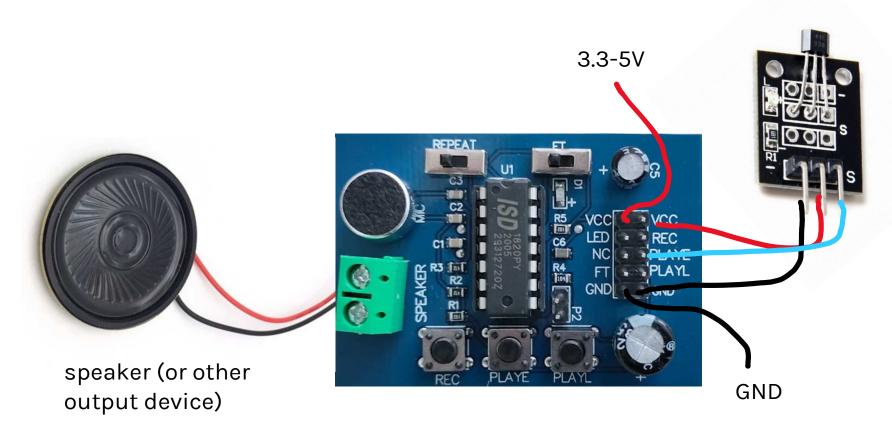

ISD1820 + hall effect sensor

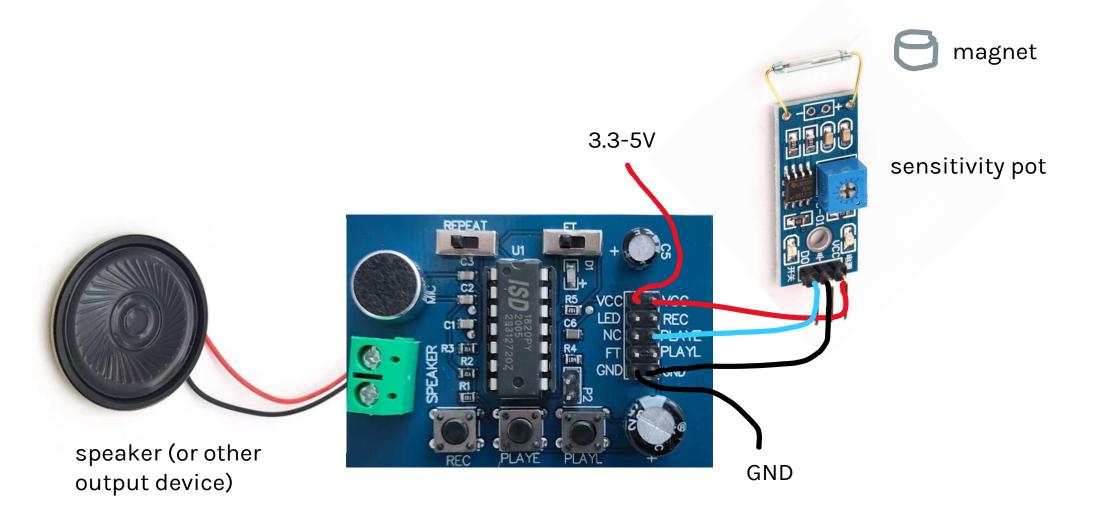

ISD1820 + reed switch

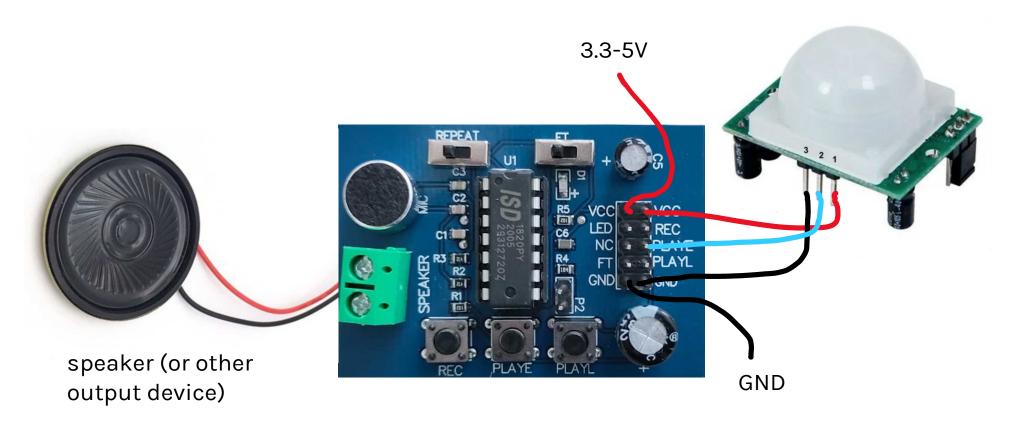

## ISD1820 + motion sensor

Needs min 4.5V (might not be reliable at 3.3V) **Tx pot** to adjust delay of trigger **Sx pot** to adjust sensitivity (distance)